



Feedback made simple

"Amplifiers oscillate and oscillators amplify!" I wanted to strangle the guy who gleefully told me that. I had been assigned to fix a perennial servo problem, and the guy who had just dumped the problem on me was dispensing cheap advice. The design was weak, and servo problems cropped up every six months. I could have stopped the oscillation with a big capacitor, but at the expense of the transient response. After careful analysis, I realized that the original designer had misapplied basic feedback theory.

In the equation for the feedback diagram, A is the

The error op amp was saturated, so to measure the phase shift, I put feedback resistors in the circuit to lower the gain.

Was this legal? Who knows?

forward gain and β is the feedback gain (Figure 1). From this equation, you can quickly come to some dramatic conclusions. When the loop gain $|A\beta| \gg 1$, the closed loop gain, V_{OUT}/V_{IN} , approaches $1/\beta$. When β is stable and predictable, as is the case with passive components, the gain is stable and predictable. If the phase shift ever exceeds -180° and if $|A\beta| \geq 1$, the circuit oscillates.

When I tried to troubleshoot the circuit, I saw big, ugly sine waves or even uglier square waves on every node I scoped. I broke the loop in an attempt to measure $A\beta$, but as soon as I did, all the circuits after the transducer (which converts position infor-

mation to voltage) saturated. Now I knew why I inherited this job; it was not going to be fun.

The transducer had -30° phase shift. The error op amp was saturated, so, to measure the phase shift, I put feedback resistors in the circuit to lower the gain. Was this legal? Who knows? But any linear measurement gives more information than a saturated circuit. The error amp had -135° phase shift at the oscillation frequency, but, even worse, the phase shift increased by another -15° . Then, a large error signal caused the amp to drive a large current into the load. Some filters and stray wiring capaci-

tance added another -20° . No wonder the servo loop oscillated: The accumulated phase shift was -200° with a loop gain greater than one.


I solved the problem by selecting a high-bandwidth op amp that could drive high-current loads with less than -115° total phase shift. This approach yielded a loop phase shift of -165° , stabilizing the system with about a 20% overshoot. I could have reduced the filter and stray-capacitance phase shift, but that would have required a board change, which management said was a no-no.

So, to design amplifiers (circuits or systems) that do not oscillate, remember the following:

- Believe me, not the data sheet. All op amps have more than -90° phase shift at the unity-gain crossover point.
- Transducers, actuators, and mechanical devices have negative phase shift.
- Driving low-impedance loads increases the amplifier's negative phase shift.
- Input-node capacitance, stray wiring capacitance, long trace lengths, and filters all add negative phase shift.

My next column will continue with feedback circuits by examining oscillators and stability.

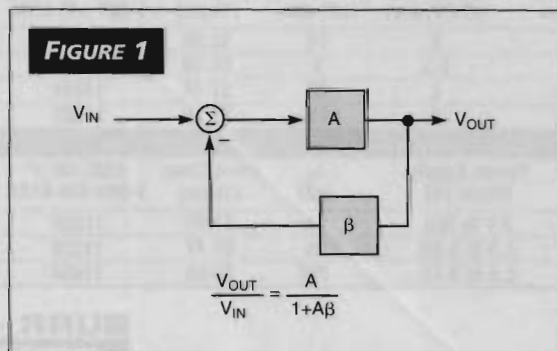Ron Mancini is a staff scientist for Harris Semiconductor (Melbourne, FL). You can reach him at 1-407-729-5171, fax 1-407-729-5069, e-mail rmancini@harris.com.



From the feedback equation, you can quickly come to some dramatic conclusions.

VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High Interest	Medium Interest	Low Interest
574	575	576